

VHDL Lab 2

Name: يوسف علي رشدي علي
ID: 23010999

Name: عبد الرحمن علي صلاح الدين
ID: 23010530

Name: علي عمرو عبدالله أحمد
ID: 23010589

Name: يوسف عاطف محمد غريب
ID: 23010993


A. Problem Statement

Design a 4-bit even/odd synchronous Counter that has an input X.

The counter should work as follows:

- If input $X = 0$, the counter counts even numbers, otherwise, it counts odd numbers.
- If counting for even numbers, the counter's value should be: 0000, 0010, 0100...
- If counting for odd numbers, the counter's value should be: 0001, 0011, 0101...

B. Simulation Samples

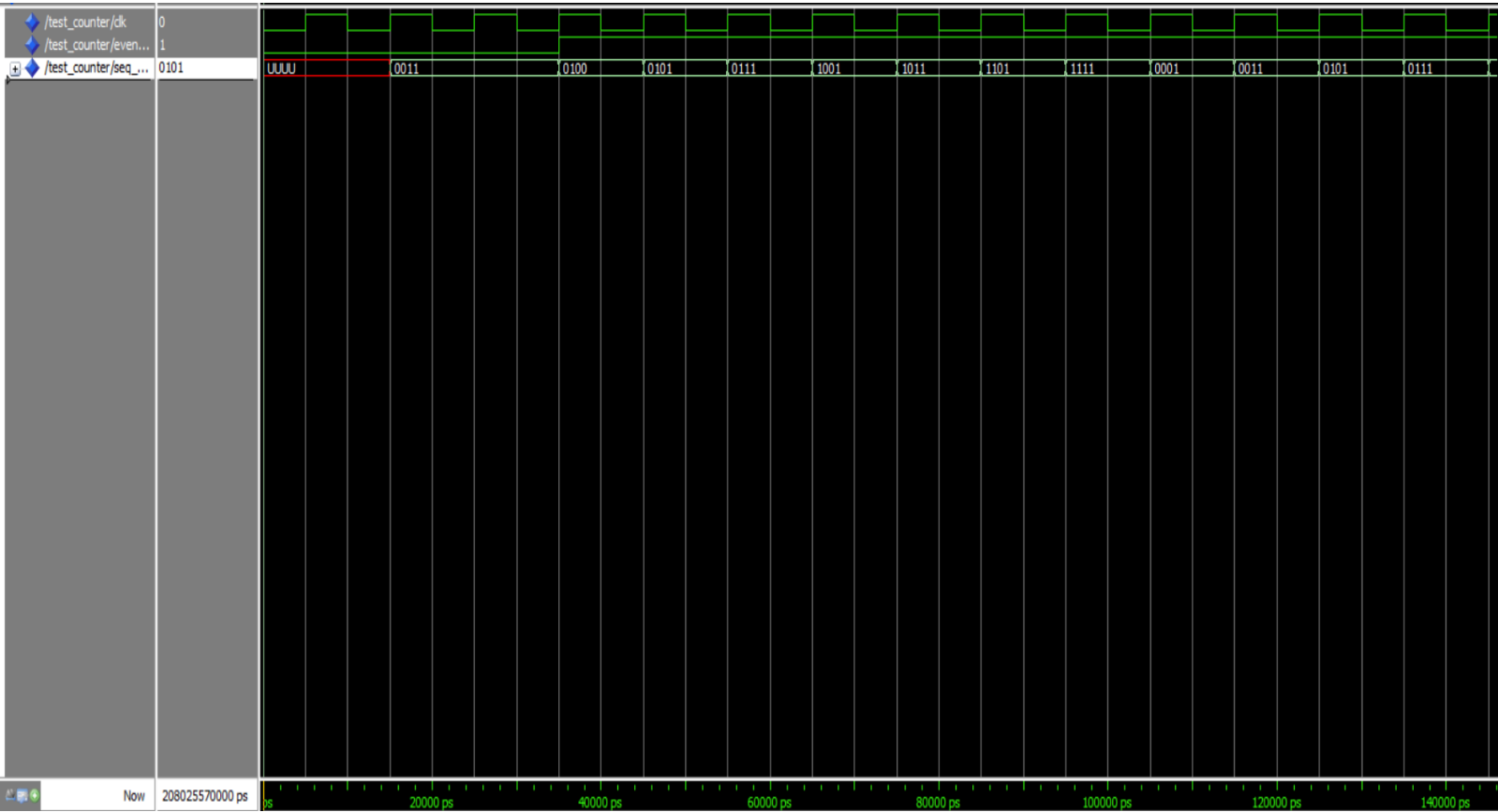


C. 1. Transition Table


Input				X = 0				X = 1			
D	C	B	A	D ⁺	C ⁺	B ⁺	A ⁺	D ⁺	C ⁺	B ⁺	A ⁺
0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	1	0	1	0	0	0	1	0	1
0	1	0	0	0	1	1	0	0	1	0	1
0	1	0	1	0	1	1	0	0	1	1	1
0	1	1	0	1	0	0	0	0	1	1	1
0	1	1	1	1	0	0	0	1	0	0	1
1	0	0	0	1	0	1	0	1	0	0	1
1	0	0	1	1	0	1	0	1	0	1	1
1	0	1	0	1	1	0	0	1	0	1	1
1	0	1	1	1	1	0	0	1	1	0	1
1	1	0	0	1	1	1	0	1	1	0	1
1	1	0	1	1	1	1	0	1	1	1	1
1	1	1	0	0	0	0	0	1	1	1	1
1	1	1	1	0	0	0	0	0	0	0	1

C. 2. State Graph

$X=0$ [Even]

 

$X=1$ [Odd]

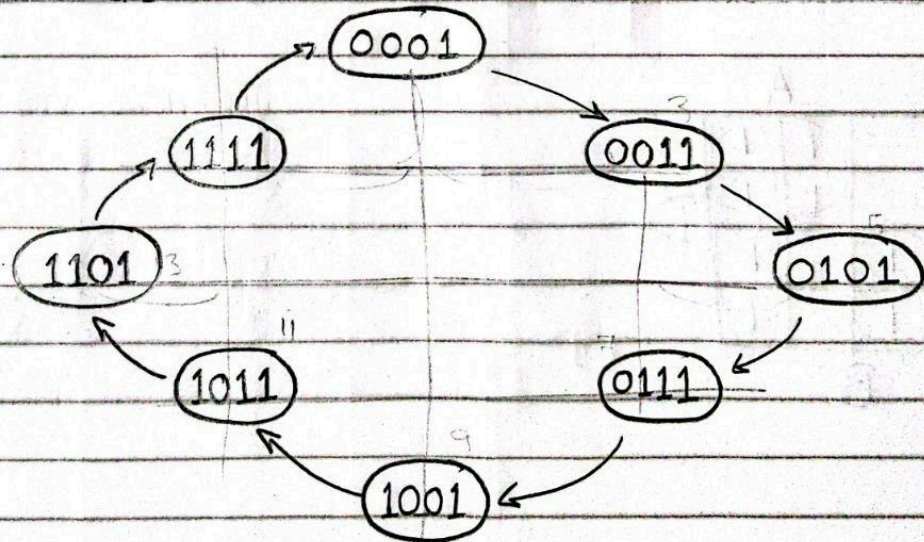

C. 3. Karnaugh Maps

<div>DC BA</div>	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

Result

$$F = 0$$

DC \ BA	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

Result

$$F = B \bar{A} + \bar{B} A$$

BA \ DC	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	0	0	0	0
10	0	0	0	0

Result

$$F = \overline{B}$$

<div> <div>DC</div> <div>BA</div> </div>	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

Result

$$F = 1$$

DC \ BA	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	1	0	1
10	0	0	1	1

Result

$$F = D\bar{C} + \bar{A}D + \bar{B}D + BA\bar{D}C$$

DC BA	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	0	0	1
10	0	1	1	0

Result

$$F = \bar{A}C + \bar{B}C + BA\bar{C}$$

DC BA	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	0	0	1
10	1	X	0	1

Result

$$F = B \bar{C} + \bar{B} C$$

<div> <div>DC</div> <div>BA</div> </div>	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	1	0	1
10	0	1	0	1

Result

$$F = D\bar{C} + \bar{B}D + B\bar{D}C$$

C. 4. Equations

$$X = 0$$

$$A^+ \Rightarrow 0$$

$$B^+ \Rightarrow \bar{C}$$

$$C^+ \Rightarrow B\bar{C} + \bar{B}C \Rightarrow B \oplus C$$

$$D^+ \Rightarrow A\bar{B} + A\bar{C} + \bar{A}BC \Rightarrow A(\bar{B}C) + \bar{A}BC \Rightarrow A \oplus (B.C)$$

$$X = 1$$



$$A^+ \Rightarrow 1$$

$$B^+ \Rightarrow C\bar{D} + \bar{C}D \Rightarrow C \oplus D$$


$$C^+ \Rightarrow B\bar{C} + B\bar{D} + \bar{B}CD \Rightarrow B(\bar{C}D) + \bar{B}CD \Rightarrow B \oplus (C.D)$$


$$D^+ \Rightarrow \bar{A}BCD + A\bar{D} + A\bar{C} + A\bar{B} \Rightarrow \bar{A}(BCD) + A(\bar{B}C\bar{D}) \Rightarrow A \oplus (B.C.D)$$

C. 5. Circuits Diagrams

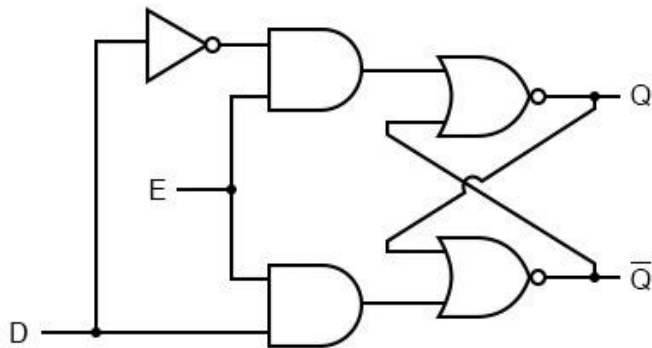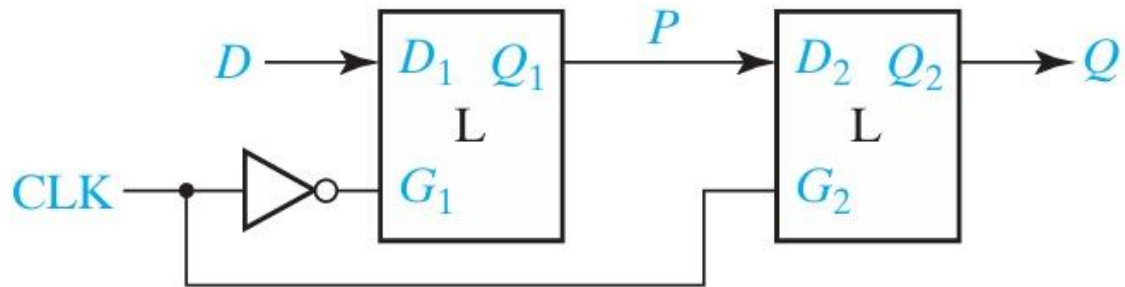

E	D	Q	\bar{Q}
0	0	latch	latch
0	1	latch	latch
1	0	0	1
1	1	1	0

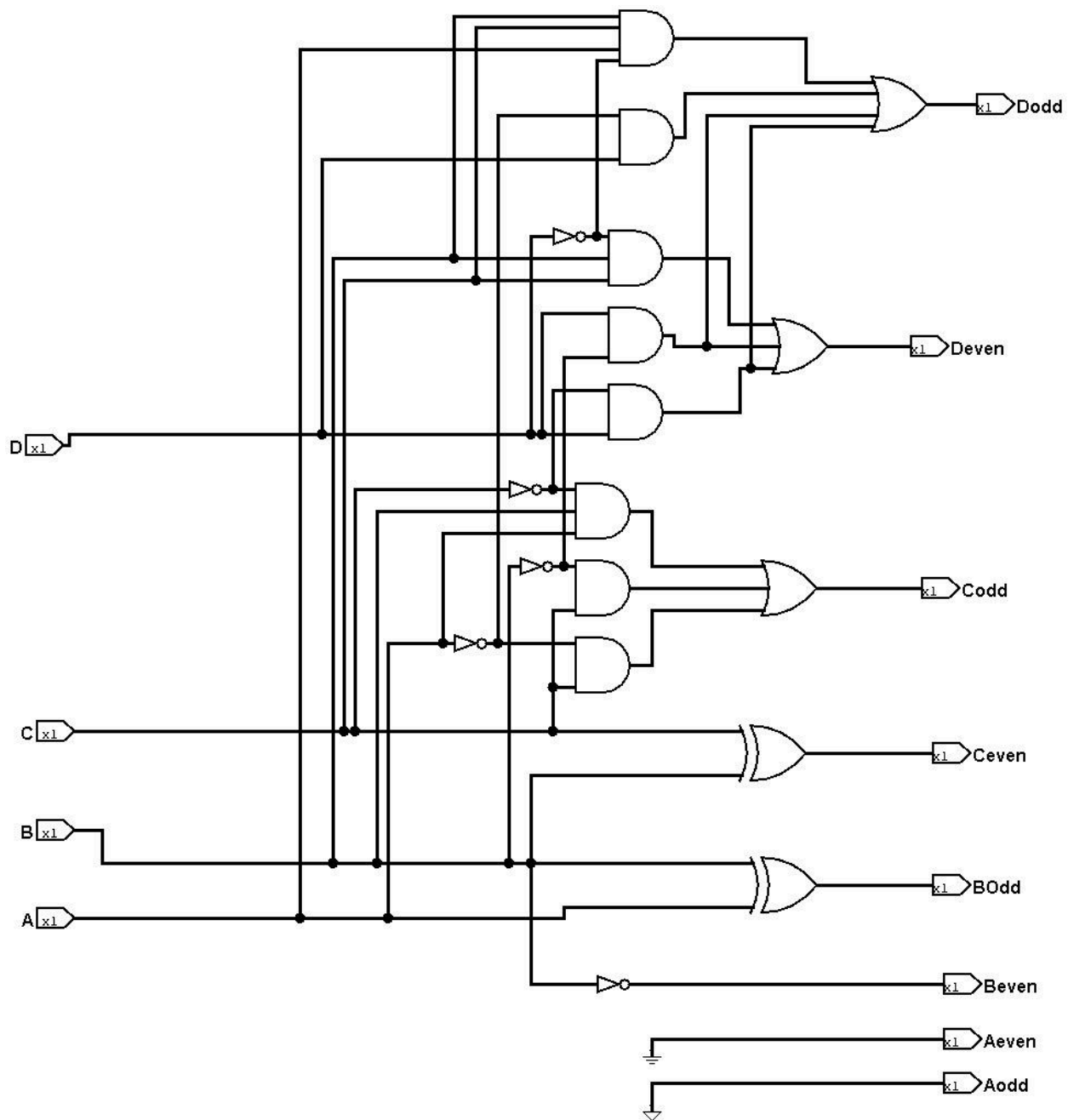

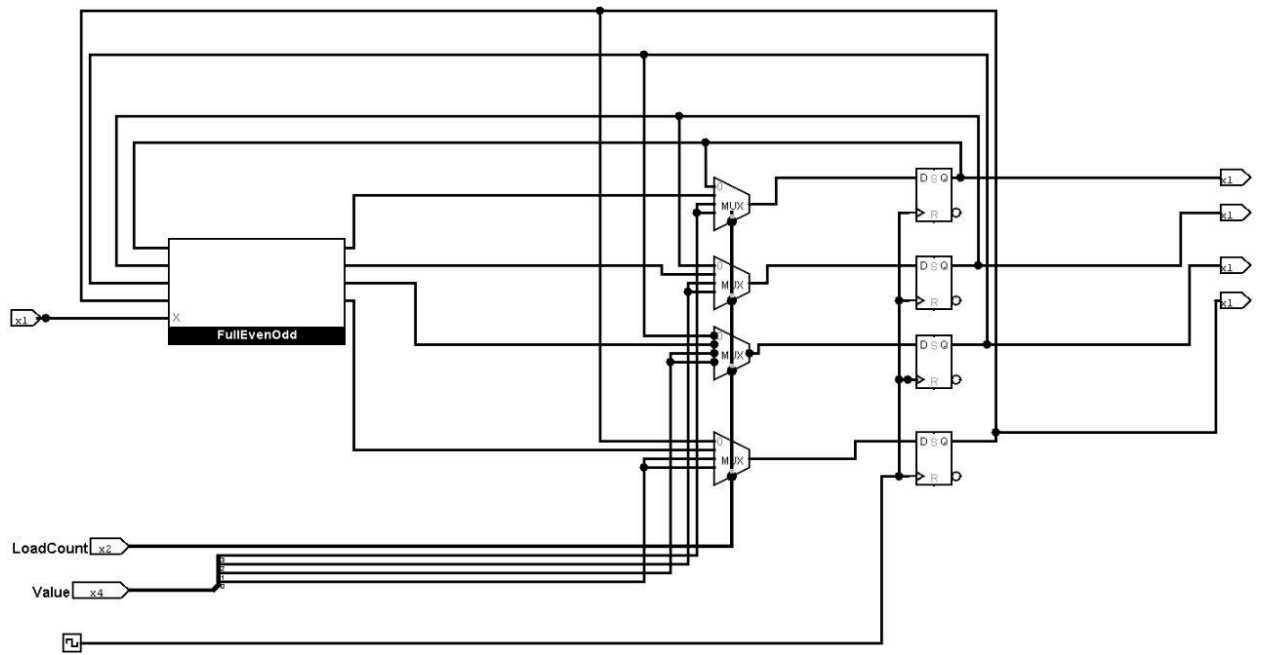

D. Assumptions

- Counter changes value on the rising edge of the clock.
- Load is prioritized over count.
- When $X = 0$, the counter is assumed to be even. If the current value is odd, it is incremented by 1 to ensure even parity.
- When $X = 1$, the counter is assumed to be odd. If the current value is even, it is incremented by 1 to ensure odd parity.